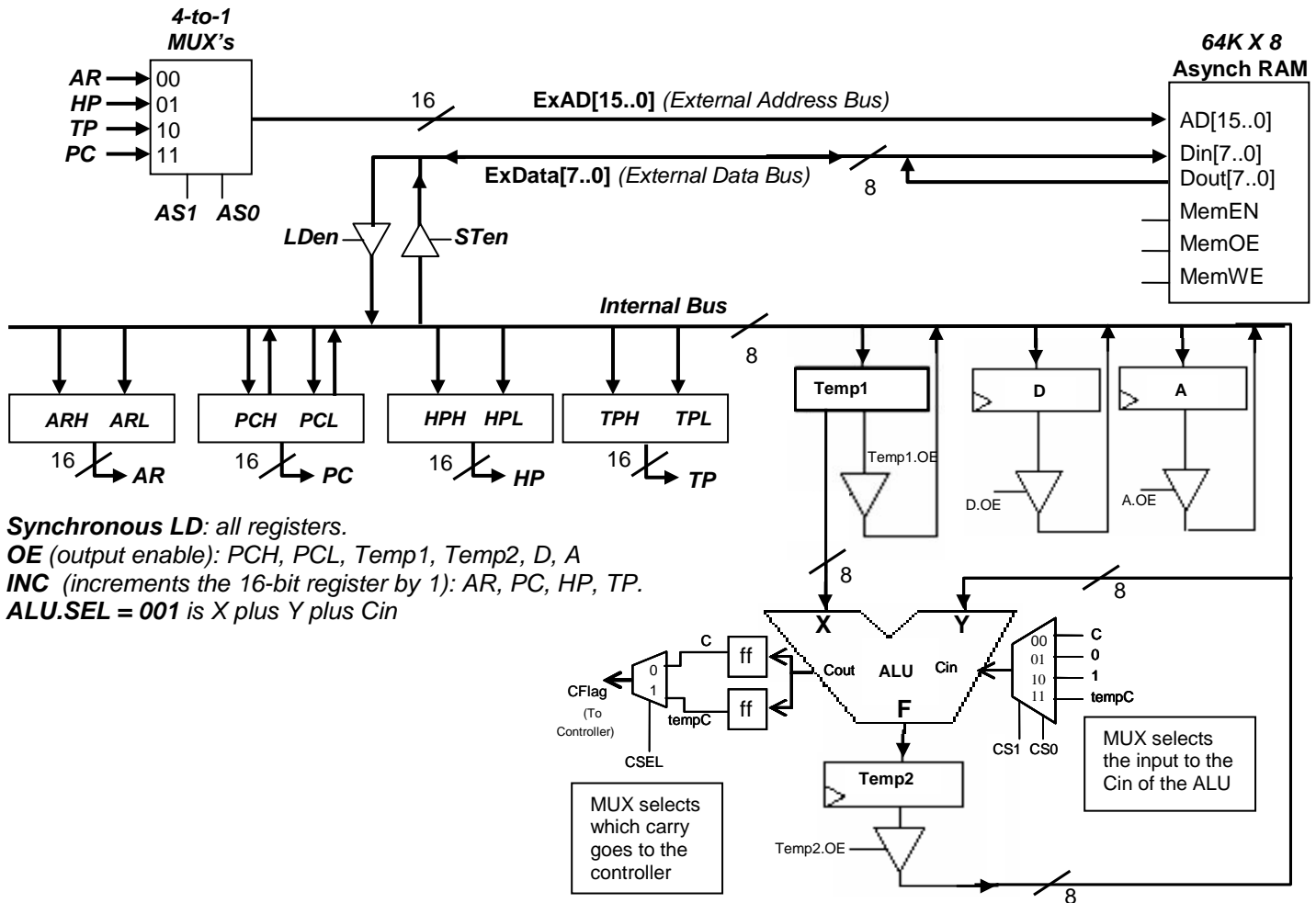



Small8-related problem: to be used for Problems 1, and 2.

Shown below is a modified architecture of the Small8 computer. Unless specified otherwise, assume that all the components are the same as you had them in your mini-project.

- HP is a 16-bit “Head” Pointer Register (HPH and HPL), containing the head of a queue. The functions of a queue will be described on the next page.
- TP is a 16-bit “Tail” Pointer Register (TPH and TPL), containing the tail of a queue. The functions of a queue will be described on the next page.
- The outputs of AR, HP, TP, and PC are connected to the External Address Bus through a set of 4-to-1 MUX's.
- The RAM is a 64K X 8 **asynchronous** RAM. The timing requirements of its read and write operations are given in the timing diagram on the next page.
- There is a new flag register called tempC (temporary carry).
- Registers Temp1 and Temp2 are connected as shown, both with a synchronous **LD** input. Temp1 also has a synchronous **CLEAR** input.



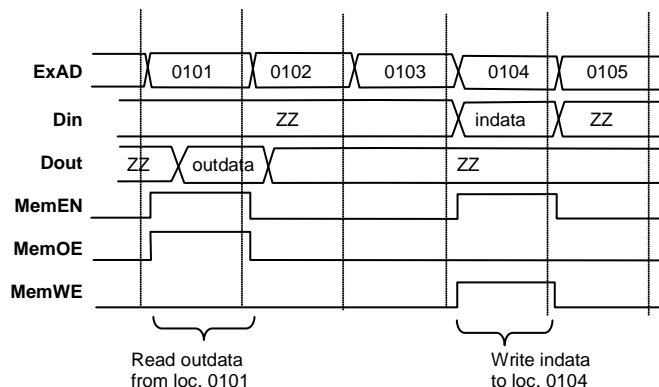Timing requirements for the read and write operations of the asynchronous RAM:




1. You are to implement three new instructions for the Small8 computer by completing the ASM chart on the next page for queue operations: LDQI \$addr, LDQA, and STAQ.

18 pts.

A stack is a “first-in, last-out” (FILO) structure. In other words, the first byte stored (pushed) onto the stack is the last byte retrieved (popped), much like a “stack” of trays in a cafeteria.

A queue, on the other hand, is a “first-in, first out” (FIFO) structure. For a queue, the first byte stored is the first to be retrieved, much like the servicing of a line of customers in a cafeteria.

 The functions (and Small8 instructions) of a queue are defined as follows:



In more detail, the Small8 instructions for queue operations are defined as follows:


Instruction	Opcode/description
LDQI \$addr	(E1) Initialize both HP and TP to the 16-bit \$addr; (This is a 3-byte instruction.) Example: LDQI \$0070 will initialize HP = \$0070 and TP = \$0070.
LDQA	(E2) Load the byte from MEM(HP) to RegA; then HP <= HP + 1. (one-byte instruction)
STAQ	(E3) Store the byte in RegA to MEM(TP); then TailPtr <= TP + 1). (one-byte instruction)

Notes:

- The queue is implemented in MEM (just like the stack in Small8).
- HP is a register containing the memory address (16 bits) of the head of the queue.
- TP is a register containing the memory address (16 bits) of the tail of the queue.
- **You don't have to worry about whether the queue is empty or full.**

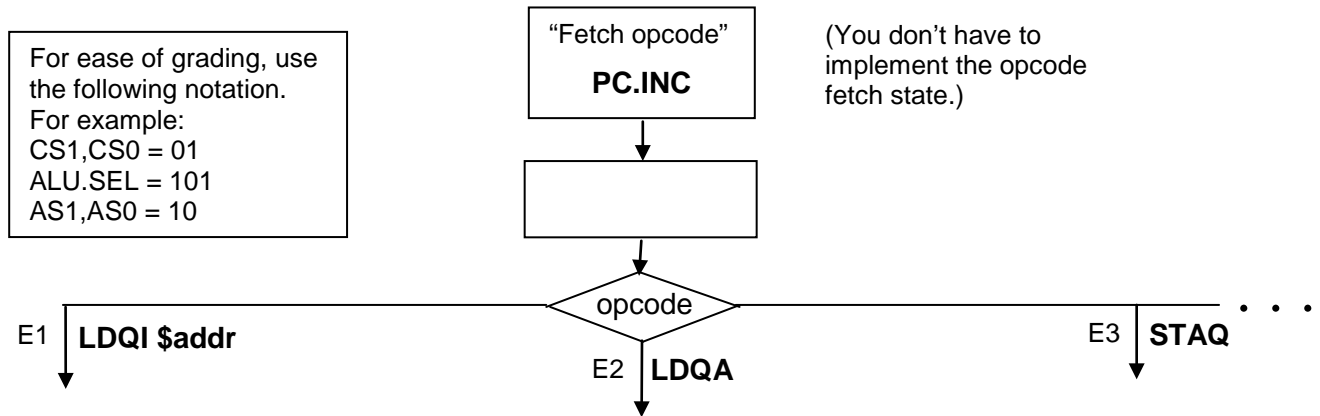1. (continued) Complete the following ASM chart. Note that you **do not** have to complete the opcode fetch state.

For maximum credit, use the minimum number of states (including the use of conditional outputs). For maximum partial credit, “comment” your ASM chart.




2. You are to implement the ADA instruction by completing the ASM chart.

20 pts.

ADA \$addr **Description:** $\text{mem}(\$addr) \leq \text{mem}(\$addr) + (A) + (C);$

- Add the content of Register A to some content in memory (in location \$addr)
- For example ADA \$0070 will add the content of Register A to memory location \$0070.
- Register A should retain its original value.
- All 4 flags are affected.

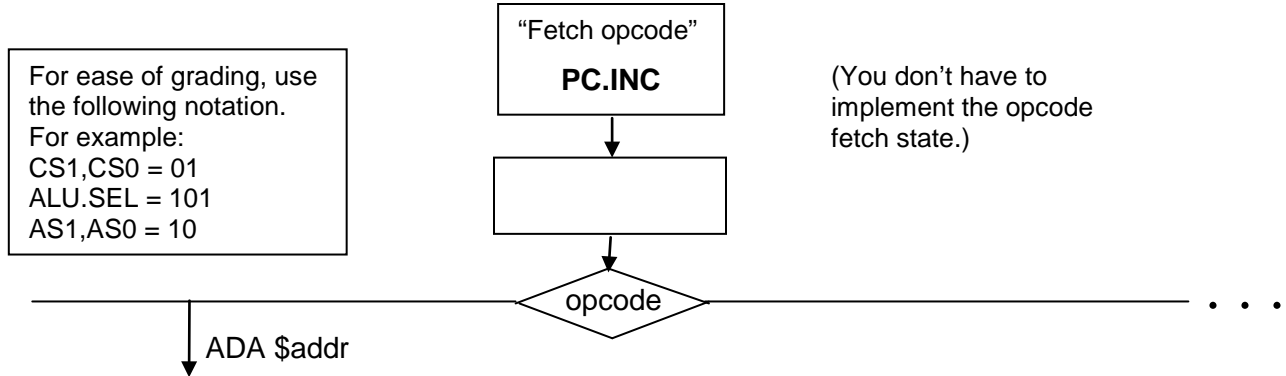For maximum credit, use the minimum number of states (including the use of conditional outputs). For maximum partial credit, “comment” your ASM chart.



3. Assembly language program and .mif file

12 pts.

- (a) Given the following .mif file, analyze it and produce the corresponding assembly language program. All addresses and contents are in hex. (4 pts)

Add-ress	Cont-ent
0000	84
0001	31
0002	F6
0003	0F
0004	00
0005	BC
0006	31
0007	31
0008	B2
0009	0C
000A	00
000B	21
000C	B5
000D	02
000E	00
000F	47

Put the corresponding assembly program here:

- (b) Assume that we add one instruction (LDAA \$0070) at the beginning of the program, what would be the resulting .mif file. Put the answer there. (8 pts)

Add-ress	Cont-ent
0000	
0001	
0002	
0003	
0004	
0005	
0006	
0007	
0008	
0009	
000A	
000B	
000C	
000D	
000E	
000F	
0010	
0011	
0012	
0013	
0014	

4. **Small8 Program Execution** – at the instruction level

18 pts.

Given below is a .mif file containing a “non-sense” program involving the **CALL** and **RET** instructions. Based on the Small8 architecture in your mini-project and the instruction set at the end of this exam, fill in the table at the bottom of this page.

(Hint: it would be best to determine the corresponding assembly program first.)

Address	Content
0000	88
0001	F1
0002	00
0003	C8
0004	07
0005	00
0006	C0
0007	EC
0008	02
0009	C0
000A	71
000B	97
000C	43

Important Notes:

The opcodes for the instructions can be found at the last page of the exam.

Initial values:

- Memory location \$00F1 = 01
- Other initial values are shown below in the table.
- If any initial value is not specified, assume it is 0.

Based on what you know about your Small 8 CPU, analyze the above .mif file and specify the content (in hex) of each of the registers and memory locations. Note that each row in the table below represents the contents at the end of the execution of each instruction. All values should be in HEX.

For ease of grading, leave the box blank to indicate no change to a register or memory location.


Initial
Values

PC	AR	SP	IX	A	D	Memory Location			
						000A	000B	000C	000D
0000	0000	000A	0009	00	00	00	00	00	00

* Fill to the end of the table (i.e., execute only 5 instructions).

12 pts.

5. Address decoding.

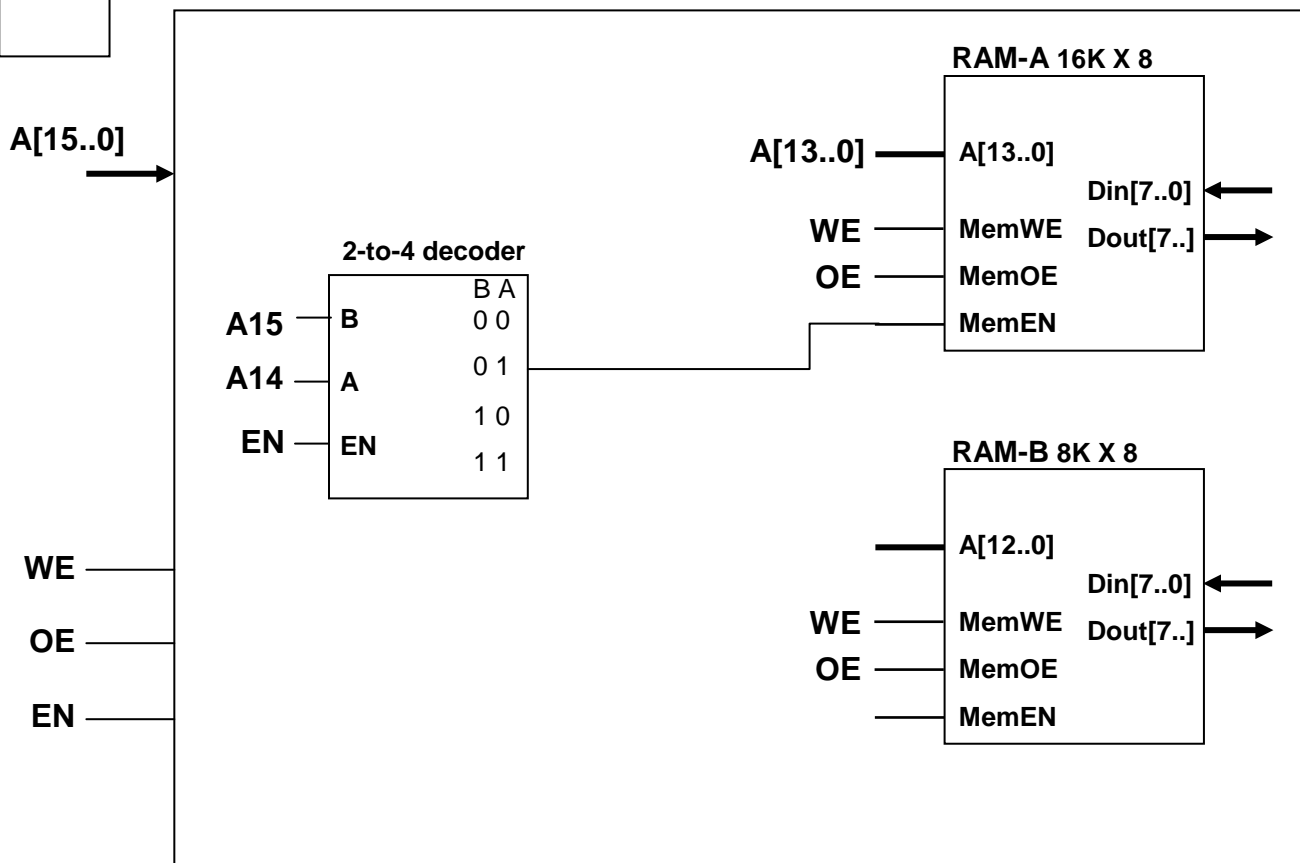

- (a) With the above connections, what is the address range of RAM-A (i.e., first and last addresses)?

For credit, show work here:

First address: _____ (in hex)

Last address: _____ (in hex)

- (c) Let's assume we change the connections as follows: A15 to A of the decoder and A14 to B of the decoder. Now, what is the address range of RAM-A?

For credit, show work here:

First address: _____ (in hex)

Last address: _____ (in hex)


- (d) **Back to the original connections** as shown in the above figure (i.e., A15 to B and A14 to A), make **ALL** the appropriate connections to make the RAM-B components to have the following range of addresses. For maximum points, use minimum number of additional gates.

(2000H – 3FFFH) and (E000H – FFFFH); i.e., each location has two addresses.

20 pts.

 6. ASM design: hardware queue component.

In Problem 1, you designed three instructions to implement and use a queue data structure in the Small8 CPU (LDQI \$addr, LDQA, STAQ). In this problem, you will design a stand-alone hardware Queue Module (nothing to do with Small8). To refresh your memory, a queue is a “first-in, first out” (FIFO) structure. For a queue, the first byte stored is the first to be retrieved, much like the servicing of a line of customers in a cafeteria.



(a) Block diagram for Queue Module

(b) Inside of the Queue Module: conceptually

The block diagram the hardware Queue Module is shown above, with two inputs: IN (8-bit input data) and OP (a 2-bit op code). It has one 8-bit output (OUT).

The functions of the Queue Module are determined by the 2-bit op code (OP):

- OP = 00 Do nothing and OUT is high-Z.
- OP = 01 Initialize Head Pointer HP = \$00 and Tail Pointer TP= \$00 (where \$00 is address \$00 of a 256X8 bit MEM)
- OP = 10 Retrieve the data byte from the queue “head”; i.e., MEM(HP) is connected to OUT as long as OP = 10; When OP changes, increment the HP register (i.e., HP \leq HP + 1).
- OP = 11 Store the data byte from IN to the queue “tail”; i.e., Mem(TP) \leq IN; then increment TP (i.e., TP \leq TP+ 1);


Notes:

The architecture to be used for the Queue Module is given on the next page (again nothing to do with Small8).

- The queue is implemented in a 256 X 8 asynchronous RAM.
- HP is a register containing the memory address (8 bits) of the head of the queue.
- TP is a register containing the memory address (8 bits) of the tail of the queue.
- You don’t have to worry about whether the queue is empty or full.

A controller will be used to control the architecture (shown on the next page) to implement the Queue Module.

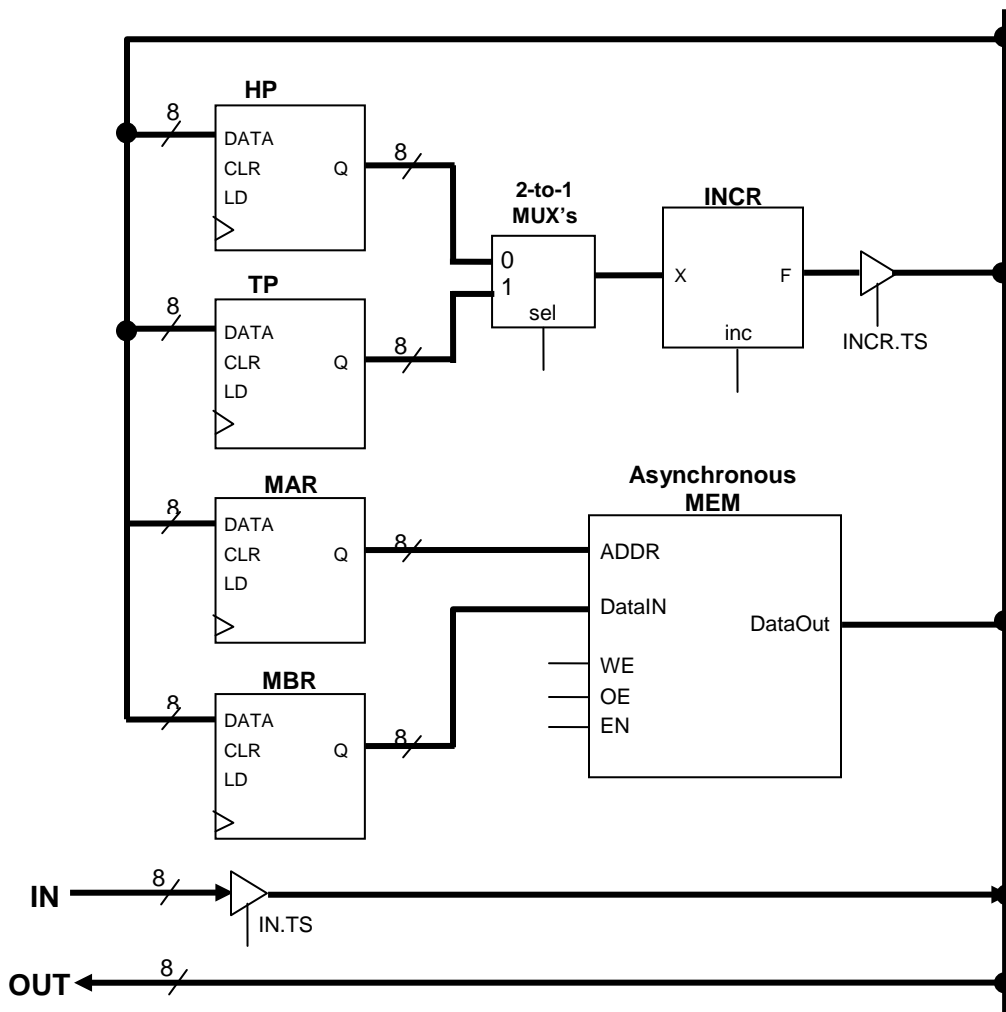For this problem, all you have to do is to design this controller (i.e., give me the ASM chart on page 10).



For the following registers: **HP, TP, MAR, MBR**:

- CLR – synchronous clear
- LD – synchronous load

For the **INCR** component:

- If inc = 0, then $F \leq X$
- If inc = 1, then $F \leq X + 1$ (i.e., increment X)

For the asynchronous MEM module:

- ADDR is an 8-bit address bus (i.e., 256 locations)
- The data bus is separated into two buses:
 - DataIN
 - DataOUT
- MEM functions as follows:

EN	OE	WE	Operation	0 = low 1 = high
0	X	X	DataOut \leq High-Z	
1	1	0	DataOut \leq MEM[Addr]	(Memory read)
1	X	1	MEM[Addr] \leq DataIn; DataOut \leq High-Z	(Memory write)

Assume that MEM is asynchronous and memory read and write can be done in 1 clock cycle.

6 (continued) Give the ASM chart necessary to implement the controller for the Queue Module.

- The best answer gets the most points.
- For partial credit, comment the function of the states and conditional outputs.

Hint: Here are the inputs and outputs of this controller.

- **Inputs:** OP, CLOCK
- **Controller outputs:** HP.CLR, HP.LD, TP.CLR, TP.LD, MAR.CLR, MAR.LD, MBR.CLR, MBR.LD, MEM.WE, MEM.OE, MEM.EN, MUX.sel, INCR,inc, INCR.TS, IN.TS

IMPORTANT:

- Please be neat and write (or draw) carefully. If we cannot read it with a reasonable effort, it is assumed wrong.
- As always, the best answer gets the most points.

COVER SHEET:

Problem: **Points:**

1 (18 pts)	
2 (20 pts)	
3 (12 pts)	
4 (18 pts)	
5 (12 pts)	
6. (20 pts)	

Total

Re-Grade Information:
